

Midterm Examination

Friday, March 3rd 2006

11:10 - 12:00 (50 minutes)

Name: Solutions _____

Student Number: _____

Q1 _____/20

Q2 _____/13

Q3 _____/7



Q4 _____/20

Q5 _____/5

Total _____/65

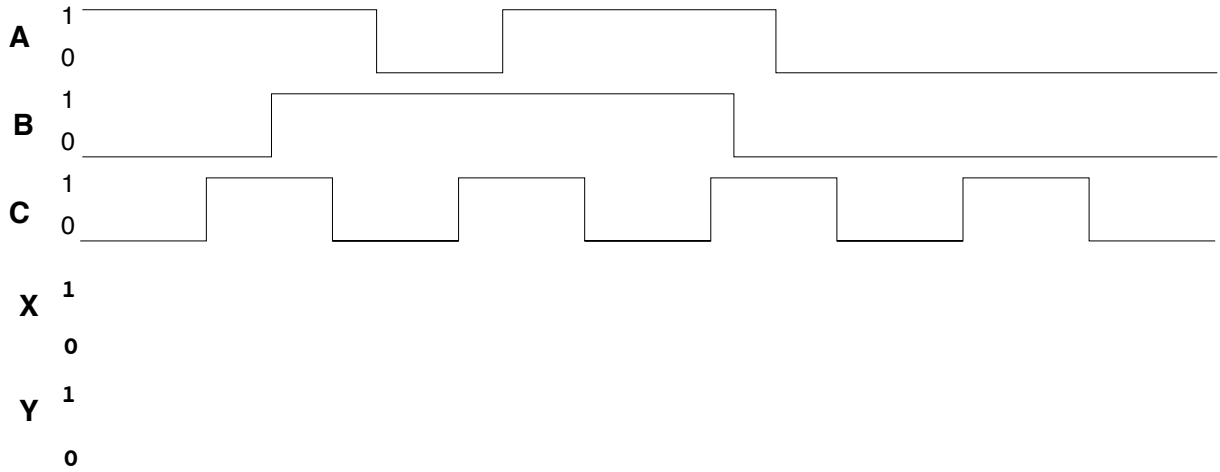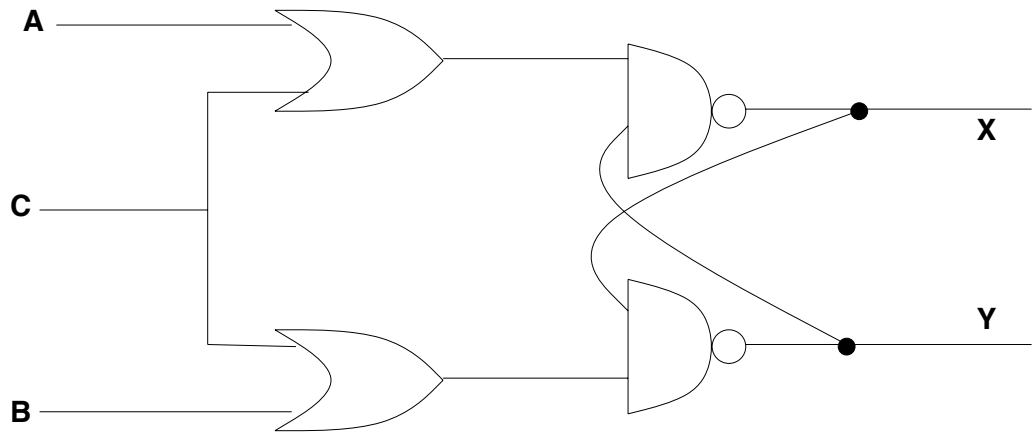Question 1 (20 marks)

Consider the circuit diagram shown below. Given the inputs A , B , and C , determine (draw) the outputs for X and Y .



Question 2 (13 marks)

Consider the 1-byte numbers 86, -38, -97.

1. What is the binary representation of 86:
 - (a) in sign and magnitude representation? (1)
 - (b) in one's complement representation? (1)
 - (c) in two's complement representation? (1)
2. What is the binary representation of -38:
 - (a) in sign and magnitude representation? (1)
 - (b) in one's complement representation? (1)
 - (c) in two's complement representation? (1)
3. What is the binary representation of -97:
 - (a) in sign and magnitude representation? (1)
 - (b) in one's complement representation? (1)
 - (c) in two's complement representation? (1)

4. Add 86 and -38 using two's complement representation.

(binary)

86

+ -38

(1)

Does it overflow?

(1)

5. Add -38 and -97 using two's complement representation.

(binary)

-38

+ -97

(1)

Does it overflow?

(1)

Question 3 (7 marks)

Prove NOR operator is NOT associative. (I.e. prove that the associative property does not hold for the NOR operator). Proof by contradiction

Question 4 (20 marks)

Consider the function $f(w, x, y, z) = w \oplus xy$ with don't care conditions $g(w, x, y, z) = \bar{w}\bar{x}$.

- Implement the function (with don't care conditions) by first minimizing it using a Karnaugh map in the space provided and writing the minimized expression in sum-of-products form (you must use the Karnaugh map and show your work). You may use any other tools (such as truth tables) to aid in this task. (10 marks)
- Given the sum of products form, you may further reduce this form or leave it as it is. Implement the circuit using one NOT gate, one 4:1 multiplexor and one two-input logic gate. (5 marks)
- Implement the resulting circuit using two two-input logic gates. (5 marks)

Question 5 (5 marks)

Implement the XOR function with as few NAND gates as possible. Note, to get full marks, you must implement the function with four NAND gates.